

## Ch 10

### Part one

## Alternating Sinusoidal Volage

### Casee of Resistor:

Voltage across resistor :  $U_R = RI$

Where :  $R$  : resis tan ce of resistor and  $I$  : int ensity of current

$U_R$  and  $i$  are in phase.

### Casee of pure coil(L):

Voltage across coil :  $U_L = Z_L I$ ;  $Z_L = L\omega$

Where :  $L$  : induc tan c of coil and  $I$  : int ensity of current

$U_L$  leads above current  $i$  by  $90^\circ$  ( $\varphi = \frac{\pi}{2} \text{ rd}$ )

### Casee of Resistive coil (L, r):

Voltage across coil :  $U_L = Z_{coil} I$ ;  $Z_{coil} = \sqrt{r^2 + (L\omega)^2}$

Where :  $L$  : induc tan c of coil and  $I$  : int ensity of current

$\omega$  : angular frequency (rd / s) and  $\omega = 2\pi f$  ( $f$  : frequency)

$r$  : resis tan ce of coil

$$\cos \varphi = \frac{r}{Z}$$

$U_L$  leads above current  $i$   $\varphi$

### Casee of capacitor C:

Voltage across capacitor :  $U_C = Z_c I$ ;  $Z_c = \frac{1}{C\omega}$

Where :  $C$  : capaci tan c of capacitor and  $I$  : int ensity of current

$\omega$  : angular frequency (rd / s) and  $\omega = 2\pi f$  ( $f$  : frequency)

$U_C$  lags behind current  $i$  by  $90^\circ$  ( $\varphi = \frac{\pi}{2} \text{ rd}$ )


### Case of RLC series circuit

Voltage across generator :  $U_G = ZI$ ;  $Z = \sqrt{R^2 + (Z_L - Z_C)^2}$

$$\cos \varphi = \frac{R}{Z}$$

The amplitude  $I_m$  of current  $i$  reaches a maximum value when the frequency  $f$  of the applied voltage is equal to a particular value  $f_0$ .

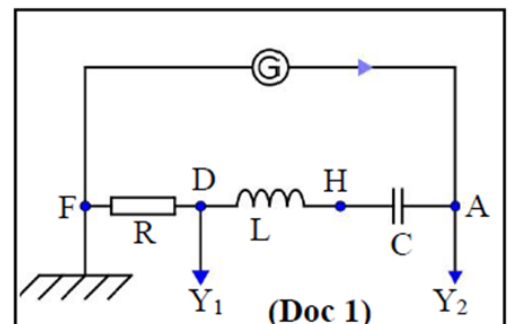$f_0$ : is called proper frequency.  $f_0 = \frac{1}{2\pi\sqrt{LC}}$



When  $f = f_0$ , the current and voltage are in phase. This phenomenon is called current resonance. So, the proper frequency is also called resonance frequency.

At resonance:  $Z_L = Z_C \Rightarrow L\omega_0^2 C = 1$

- When  $f < f_0$  (below resonance), the current leads the voltage by  $\phi$ , then circuit is capacitive.
- When  $f = f_0$  (resonance), the current and voltage are in phase  $\phi=0$ , then circuit is resistive.
- When  $f > f_0$  (above resonance), the current lags behind the voltage by  $\phi$ , then circuit is inductive.

Remark:

In case of RLC series circuit:  $U_G = \sqrt{U_R^2 + (U_L - U_C)^2}$

In case of RL series circuit:  $U_G = \sqrt{U_R^2 + U_L^2}$

In case of RC series circuit:  $U_G = \sqrt{U_R^2 + U_C^2}$

$u_G = U_m \sin(\omega t)$  and  $i = I_m \sin(\omega t + \phi)$

Power:  $P = U \cdot I \cdot \cos \phi$

where:  $U = \frac{U_m}{\sqrt{2}}$  And  $I = \frac{I_m}{\sqrt{2}}$

$U_m$  is the max voltage and  $U$  is the effective voltage.

$I_m$  is the max current, and  $I$  is the effective current.

$\Phi$  is the phase difference.

## Part 2

### Charging and Discharging a Capacitor

**Charge of capacitor:  $q = CV$  OR  $Q = CU$**

Where:

C: Capacitance of a capacitor (Unit in SI system is Farad: F)

Q or q: charge (quantity of electricity) of the capacitor (Unit in SI system is Coulomb: C)

U or u: voltage across the terminals of a capacitor. (Volt: V)

**Energy stored in a capacitor:**

$W = \frac{1}{2}CU^2$  or  $W = \frac{1}{2}QU$  or  $W = \frac{1}{2}\frac{Q^2}{C}$ . W is expressed in Joules (J).


#### ❖ Charging of capacitor:

**Differential equation:**  $E = RC \frac{du_C}{dt} + u_C$

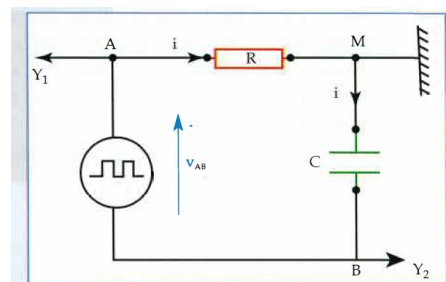
**Solution of the differential equation:**

$u_C = E(1 - e^{-\frac{t}{\tau}})$  where  $\tau = RC$  is time constant t.

after  $t = \tau \Rightarrow u_C = E(1 - e^{-\frac{\tau}{\tau}}) \Rightarrow u_C = E(1 - e^{-1}) = 0.63E$



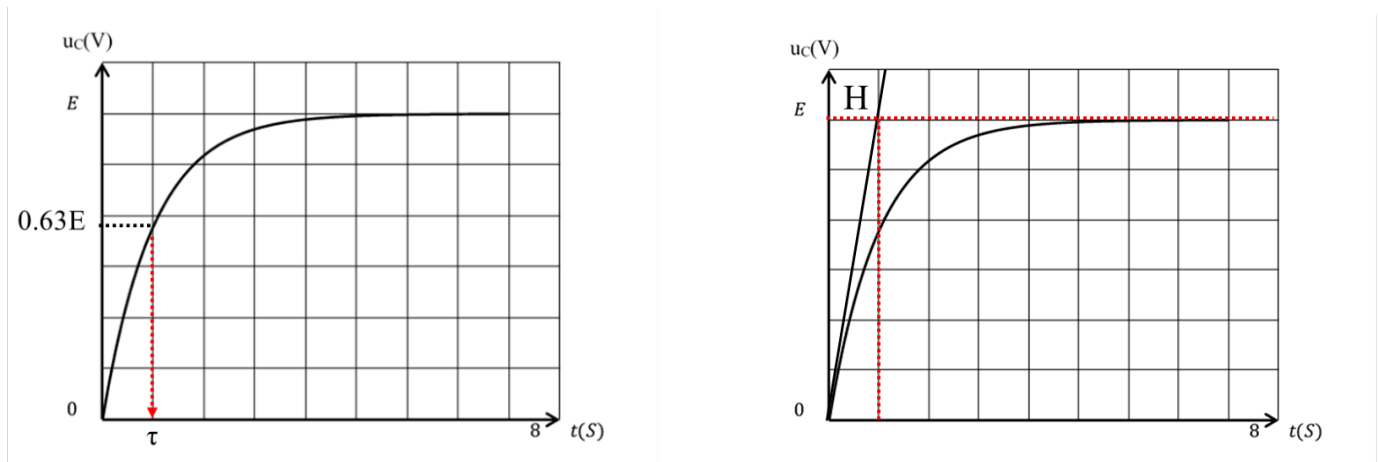Time constant  $\tau$  is the interval of time after which the voltage across the capacitor reaches 63% of its maximum value during charging of the capacitor.



after  $t = 5\tau \Rightarrow u_C = E(1 - e^{-\frac{5\tau}{\tau}}) \Rightarrow u_C = E(1 - e^{-5}) = 0.99E \approx E$

After  $t = 5\tau$ , the capacitor is practically completely charged

The tangent to  $u_C$  at  $t=0$ , meets the asymptote in a point of abscissa  $\tau$ .

### ❖ Discharging of capacitor

**Differential equation:**  $RC \frac{du_C}{dt} + u_C = 0$

**Solution of the differential equation:**  $u_C = E e^{-\frac{t}{\tau}}$  where  $\tau = RC$  is time constant.

after  $t = \tau \Rightarrow u_C = E e^{-\frac{\tau}{\tau}} \Rightarrow u_C = E e^{-1} = 0.37E$

**Time constant  $\tau$  is the interval of time after which the voltage across the capacitor reaches 37% of its maximum value during discharging of the capacitor.**

after  $t = 5\tau \Rightarrow u_C = E e^{-\frac{5\tau}{\tau}} \Rightarrow u_C = E e^{-5} = 0.006E \approx 0$

After  $t = 5\tau$ , the capacitor is practically completely discharged.

The tangent to  $u_C$  at  $t=0$ , meets the asymptote in a point of abscissa  $\tau$ .

